

# CSE460: VLSI Design

## Section 04

### Assignment 03 (Lab)

**Deadline: 16.08.22**

---

#### Rules:

You need to submit the schematic diagrams drawn on dsch2 window, timing diagrams and screenshots of some simulation results. Write a brief description explaining the results for each of the problems.

#### Problems:

1. Consider the following logic function,

$$Y = ((A + B) C) + D$$

Implement the given function on dsch2 using CMOS logic & show the corresponding timing diagram.


[Hint: You should use “clock” as input for A, B, C & D.]

2. Refer to your **lab sheet of experiment 5**.

In class, we have successfully implemented a negative edge-triggered D flip-flop. For this problem, you need to successfully implement the **negative edge-triggered D flip-flop** once again. After that, you need to construct a **controller block** and **connect with the flip-flop** to make a **D flip-flop with set-reset operations**. Finally with the designed block, you need to **implement a 4 bit Johnson counter**.

[Hint: The controller circuit, the connection between controller & D flip-flop block and the Johnson counter circuit are given on your **lab sheet**.]

 Show the corresponding timing diagram of the Johnson counter. Your output should be something like this.



**\*\*\*Complete the assignment by yourself. Copying will be strictly dealt with.**